



KIDS CORNER HAPPY INTER COLLEGE

FIROZABAD

Dear, Students complete this work and bring it when school opens.

For class 12th

Date :
Page :

Computer Project work
For class XII

Design the logic Gate? with Truth table and symbol.

Drive the Truth table to the given equation or expression

$$F = xyz + \bar{x}y + x\bar{y}$$

Find the value of F ($x=1, y=0$)

by: MD Shohinur